
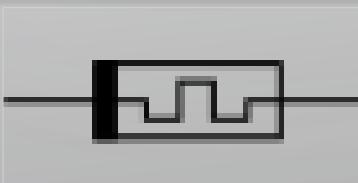


MEMRISTOR EMULATOR

THAI NGHIEM & SEAMUS PLUNKETT

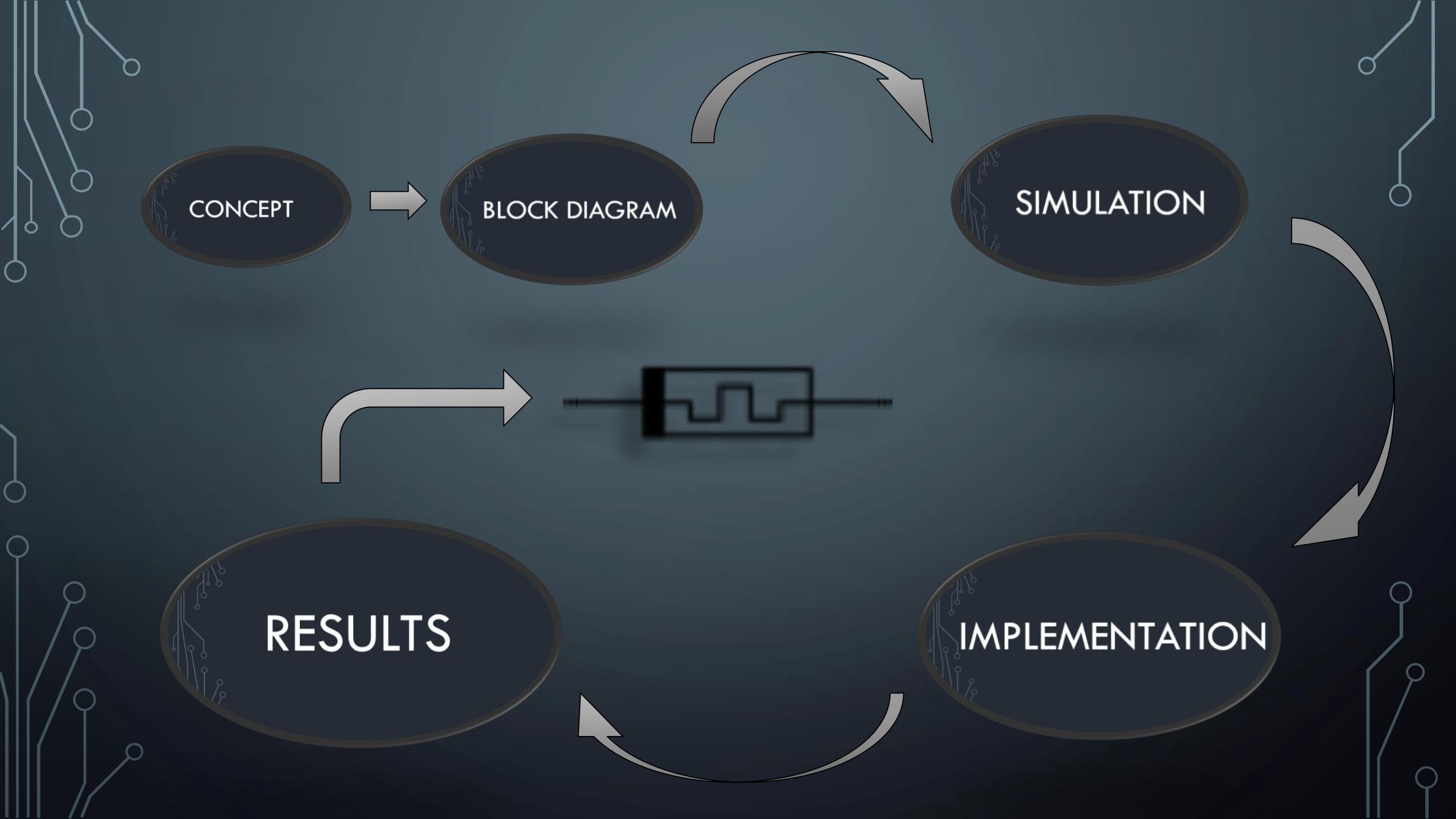





CONCEPT

THEORY

$$i(t) = W(\varphi(t))v(t),$$

where

$$W(\varphi) \equiv dq(\varphi)/d\varphi.$$

- Realize the input voltage as flux (φ)
→ Integrator
- Emulates the memristive response
→ remotely control a variable resistor
→ Light Dependent Resistor

OPTOCOUPLER


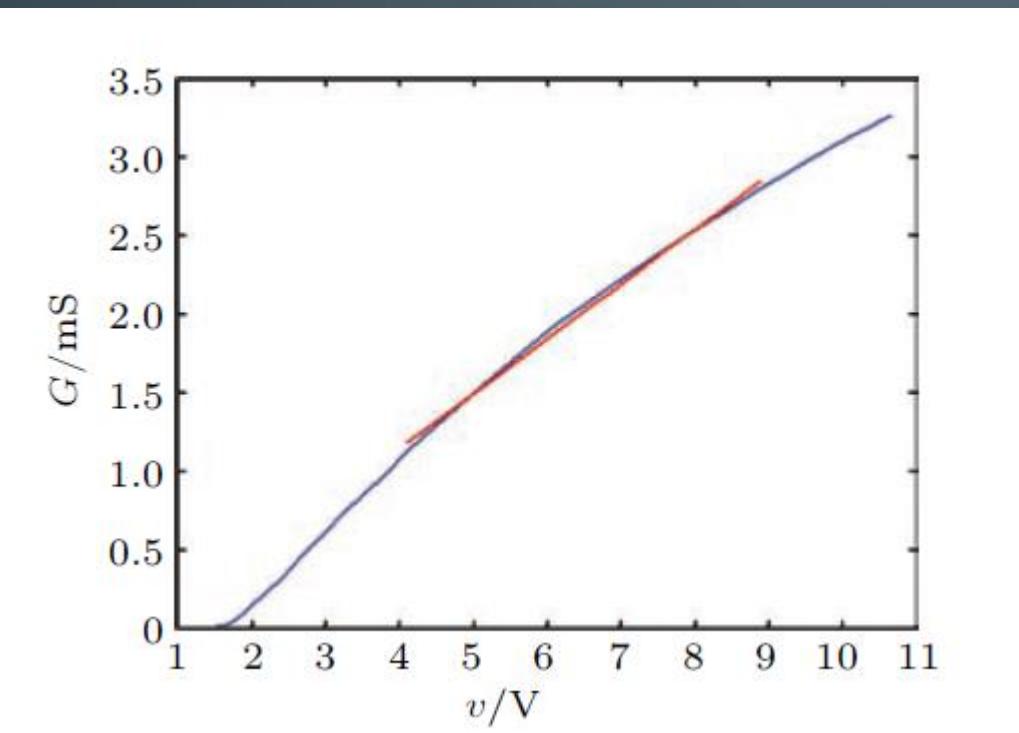


Fig. Voltage/conductance characteristics of the Silonex NSL-32.

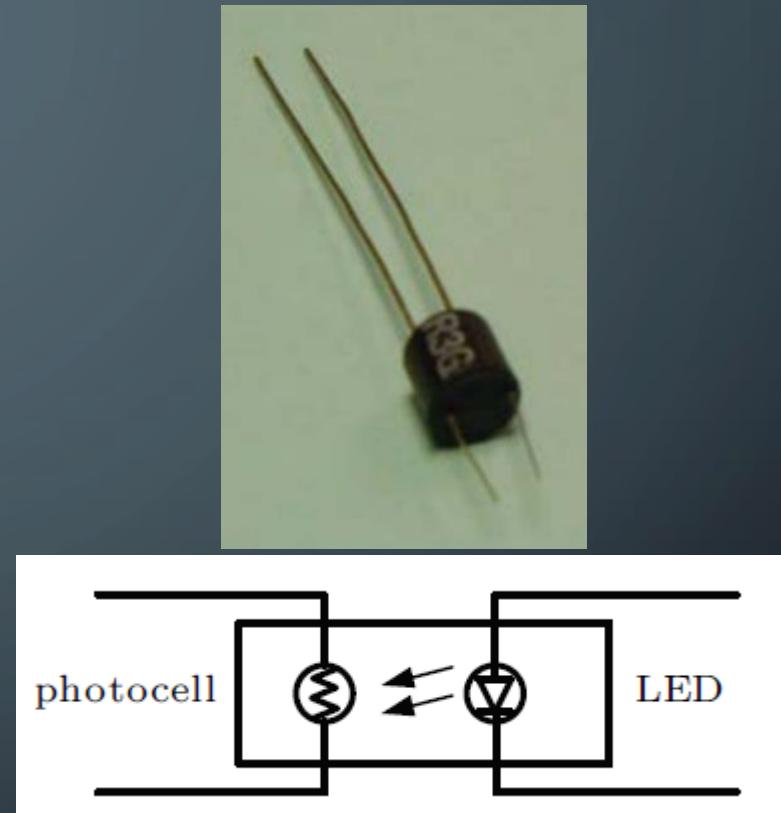


OPTOCOUPLED CIRCUITS

$$W(v) = 0.3v + 0.11.$$

- Ensure optocoupler operate in linear region
→ Summing Op-amp
- Minimize current draw from the input signal
→ Inverting Buffer


BLOCK DIAGRAM


BLOCK DIAGRAM

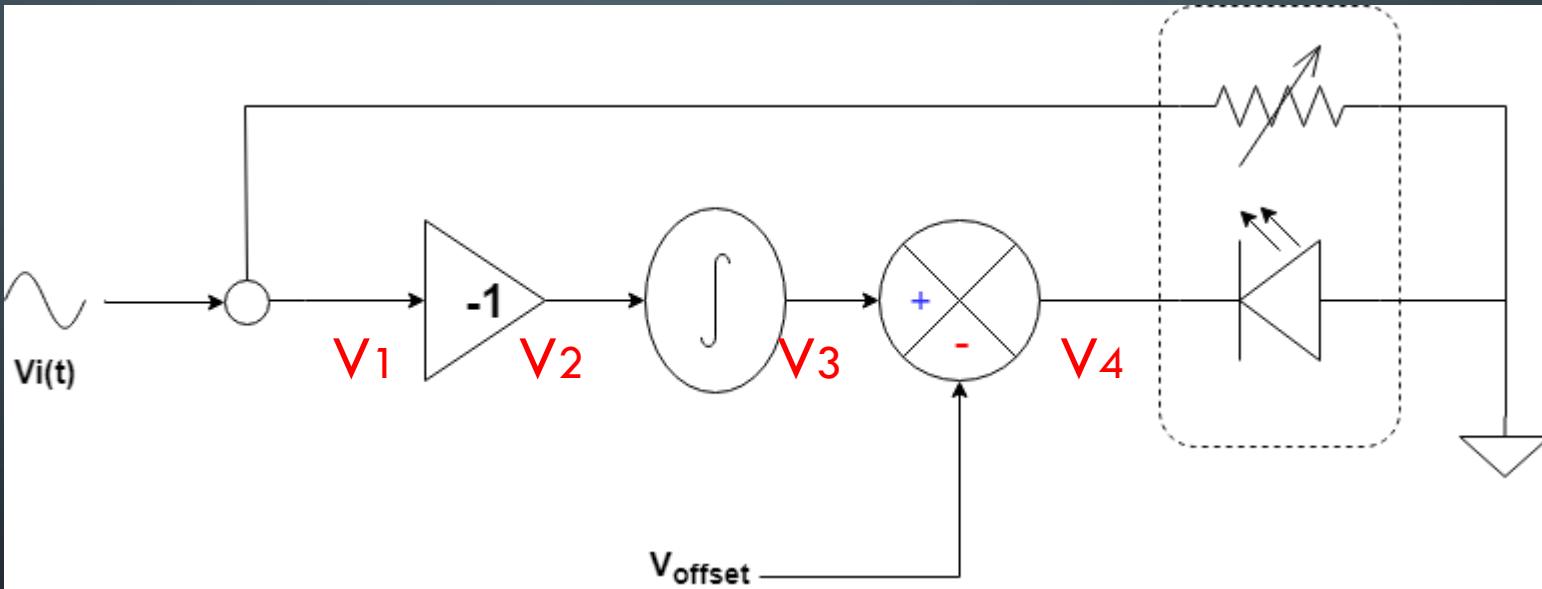



SIMULATION

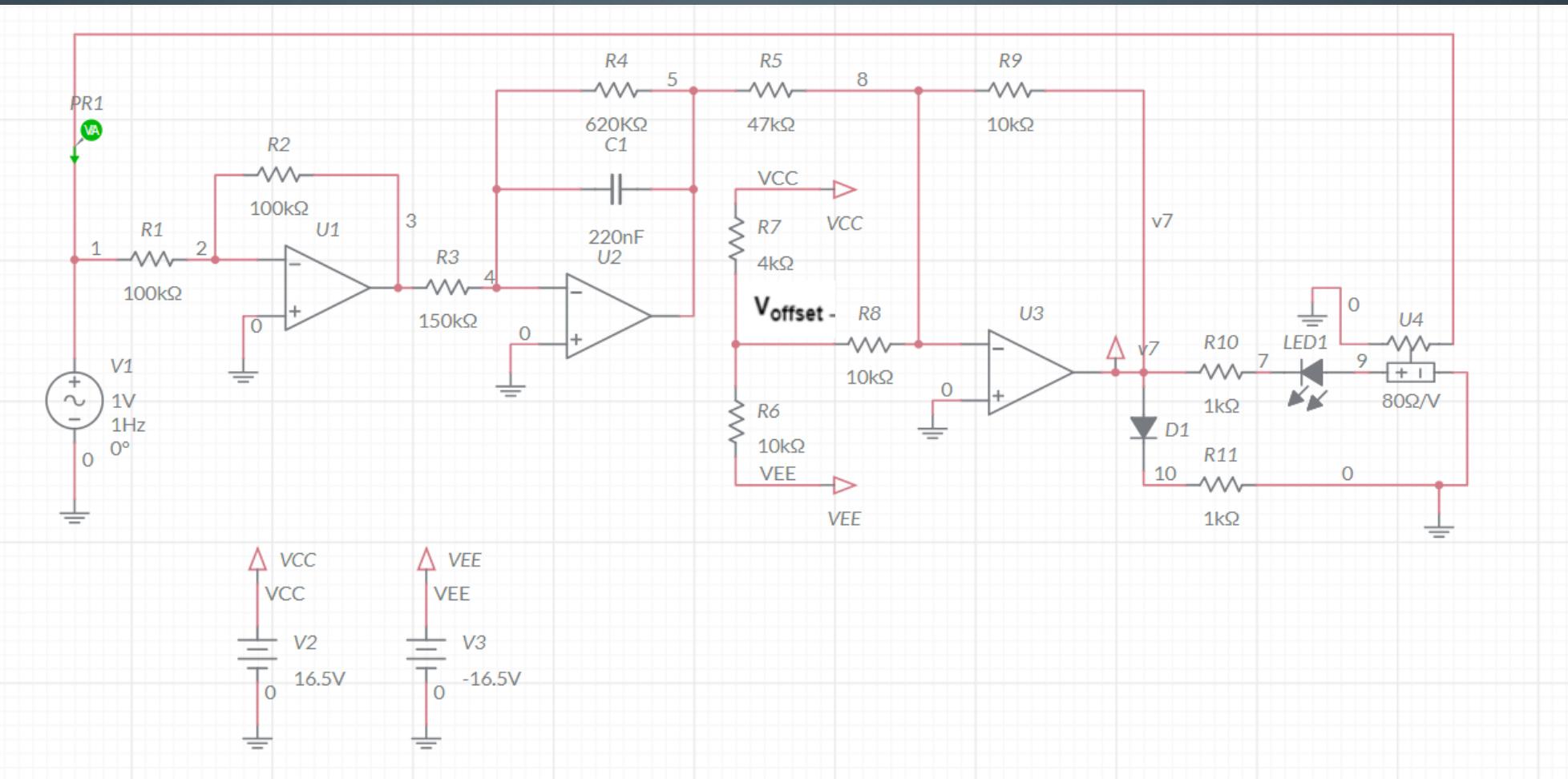

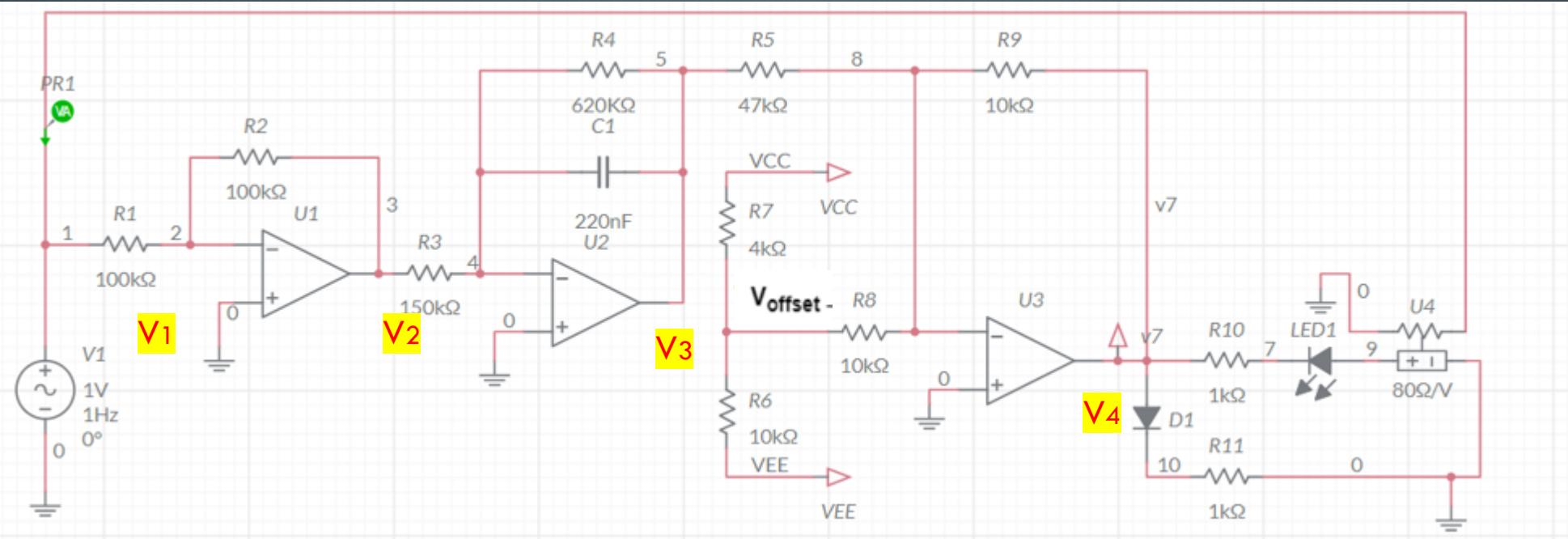


$$1) V_{1(t)} = V * \sin(\omega t)$$

$$2) V_{2(t)} = -\frac{R_2}{R_1} * V_{1(t)}$$

$$3) V_{3(t)} = -\frac{1}{R_3*C_1} * \int V_{2(t)} * dt$$

$$4) V_{4(t)} = -\frac{R_9}{R_5} * V_{3(t)} - \frac{R_9}{R_8} * V_{offset}$$

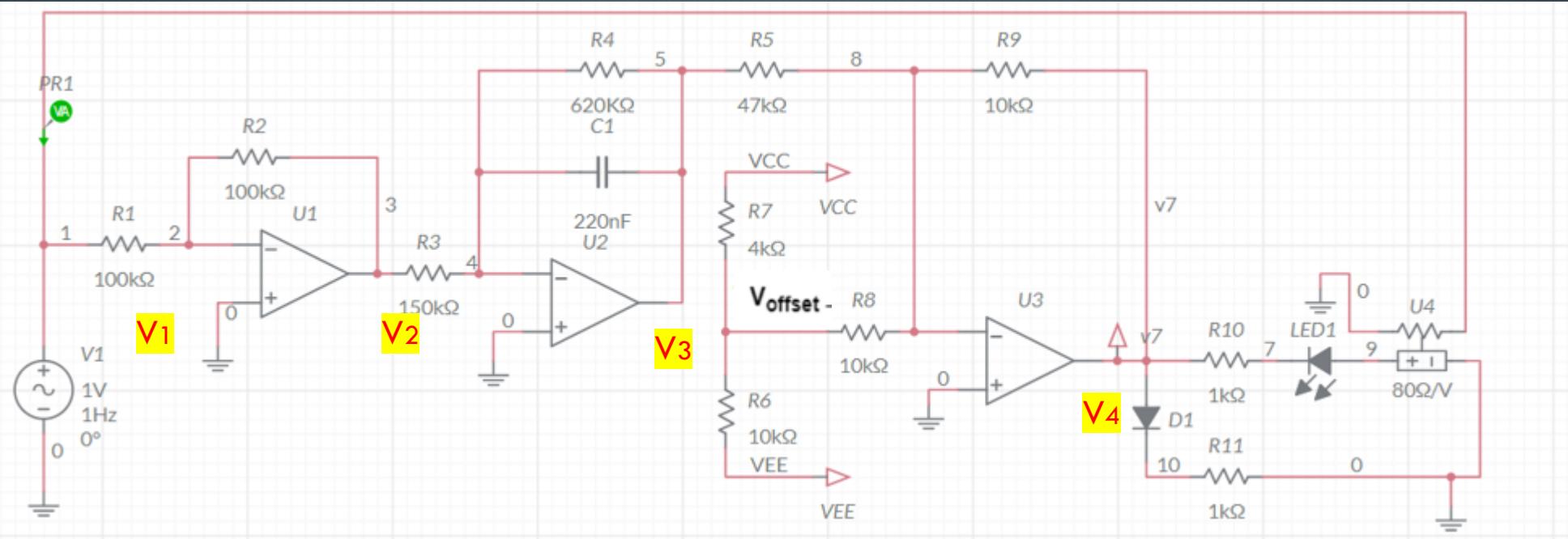
$$\boxed{V_{4(t)} = \frac{R_9 R_2 V}{w R_5 R_3 R_1 C_1} * \cos(\omega t) - \frac{R_9}{R_8} * V_{offset}}$$



$$V_{4(t)} = -\frac{R_9 R_2 V}{w R_5 R_3 R_1 C_1} * \cos(wt) - \frac{R_9}{R_8} * V_{offset}$$

$$W(v) = 0.3v + 0.11.$$
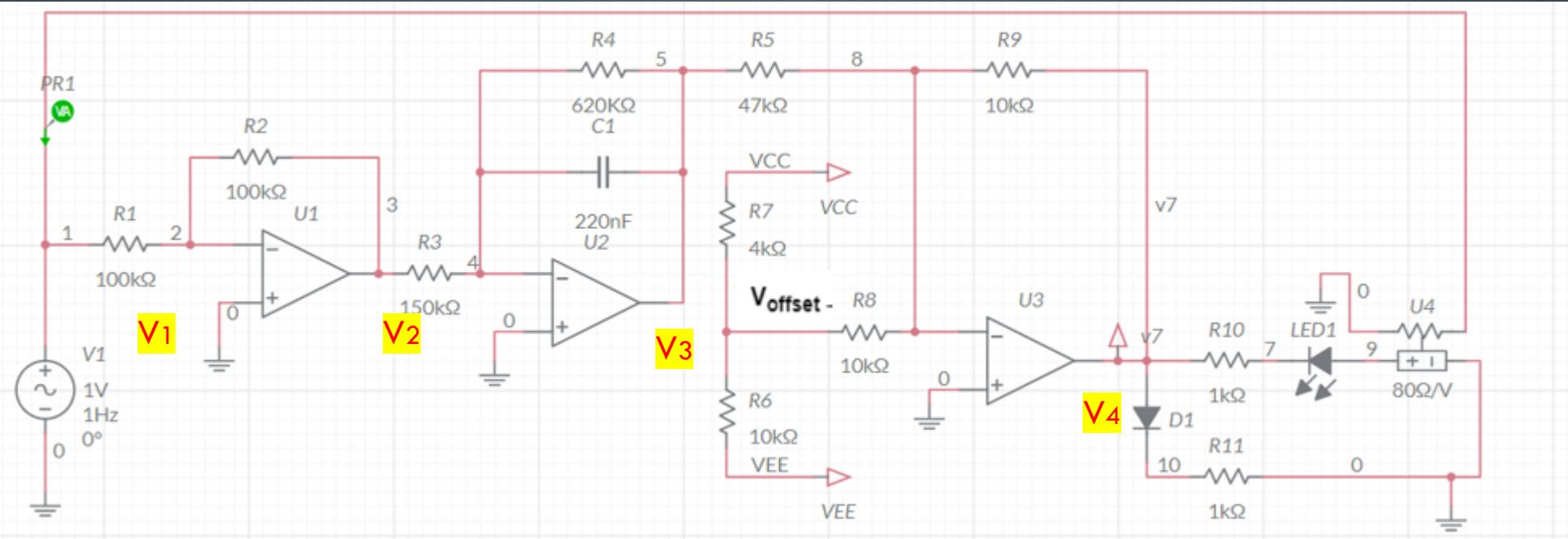
$$W_{(t)} = 0.3 * \left(0 - \frac{R_9 R_2 V}{w R_5 R_3 R_1 C_1} * \cos(wt) + \frac{R_9}{R_8} * V_{offset} \right) + 0.11$$





$$V = 1V$$

$$w = 2\pi$$

$$W(t) = 0.3 * \left(0 - \frac{V_1(t) R_2}{w R_5 R_3 R_1 C_1} * \frac{1}{V} * \sin(2\pi w t) + \frac{1}{R_8} * V_{offset} \right) + 0.11$$



IMPLEMENTATION

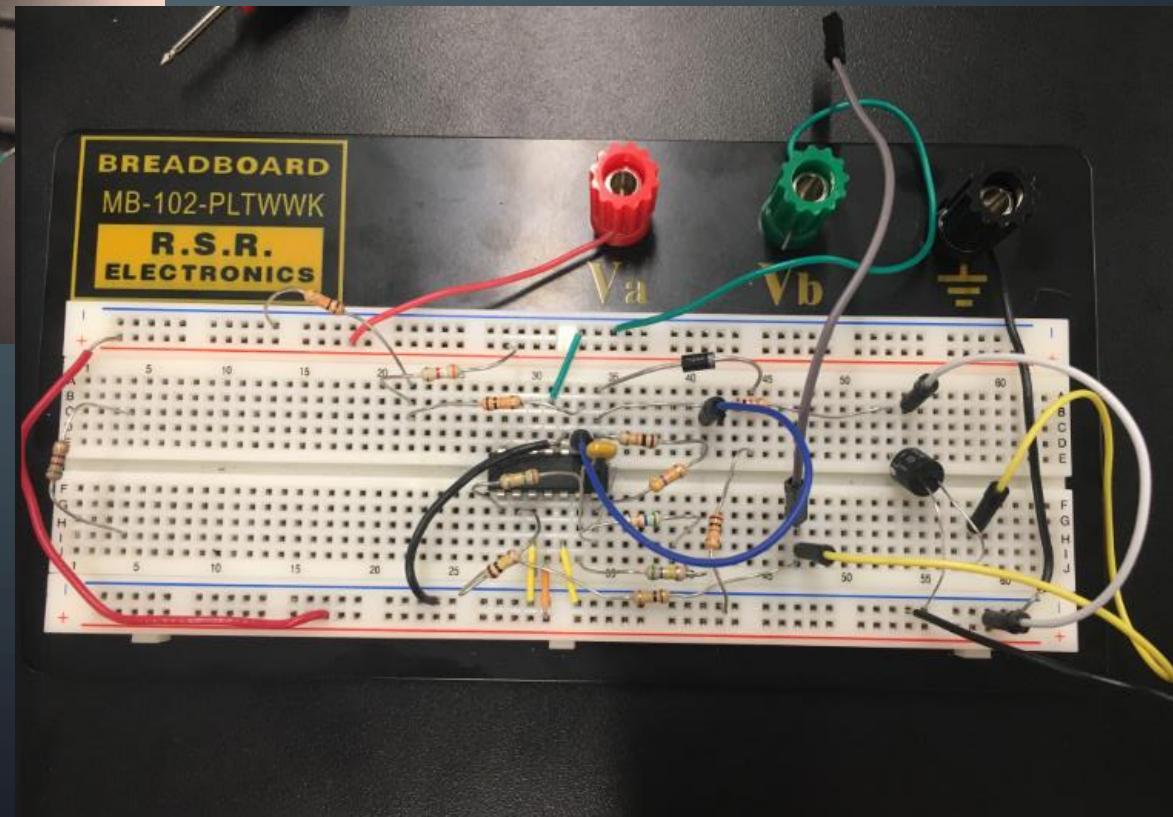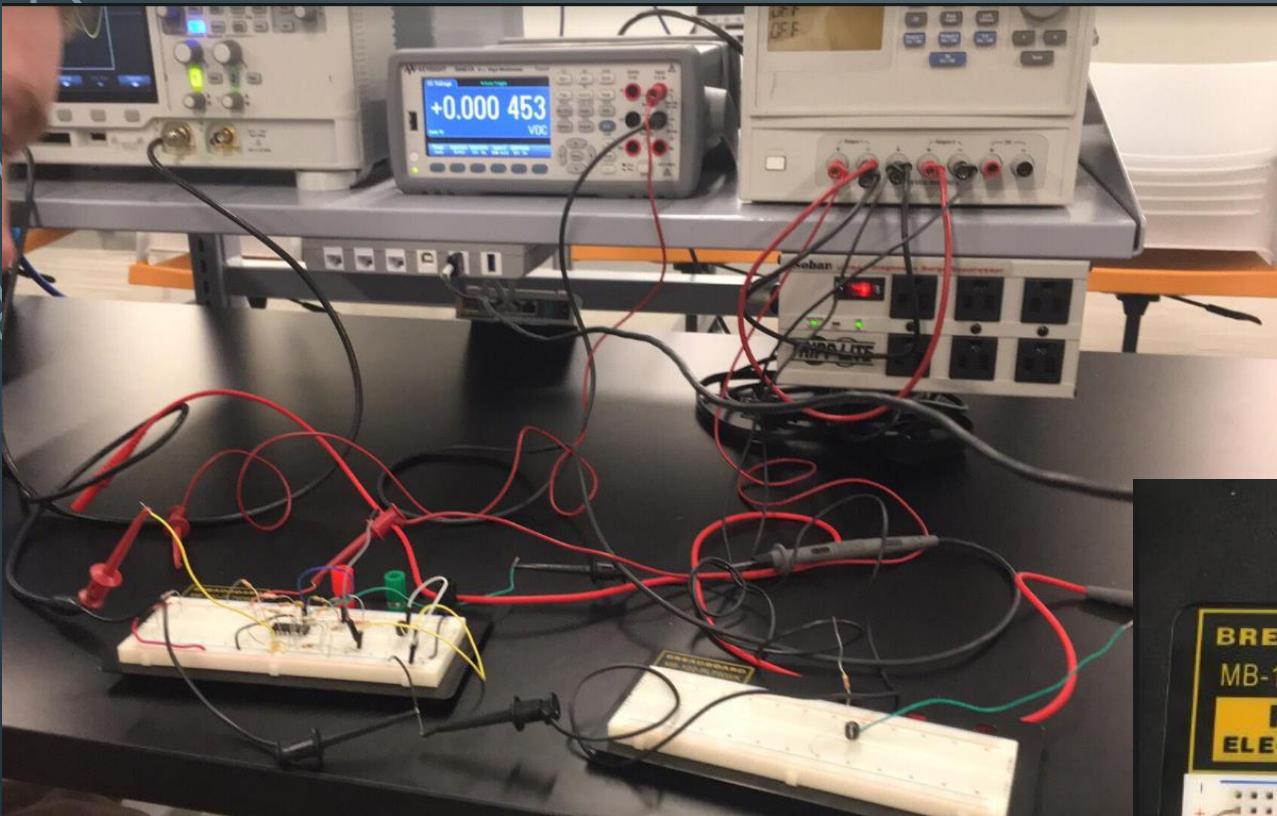



RESULTS

SIMULATION


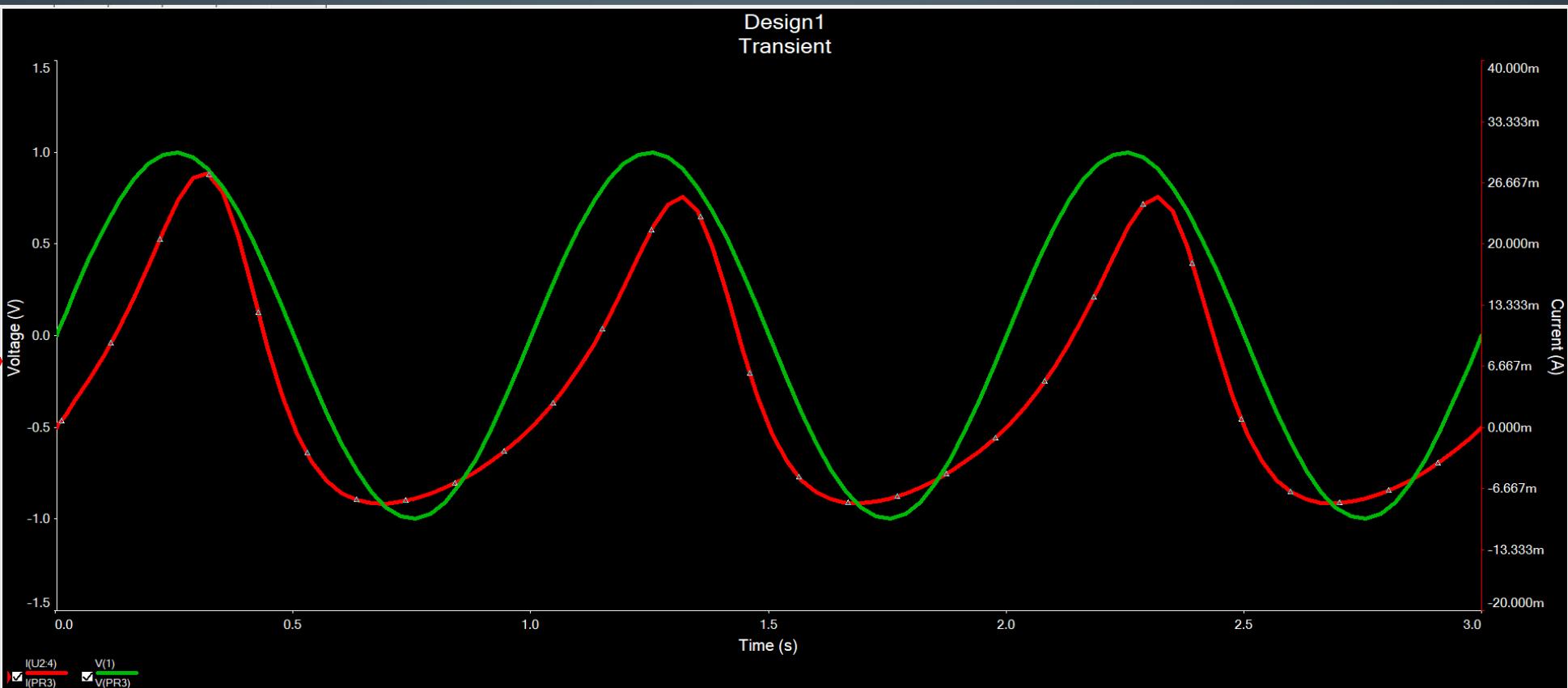



Fig. Voltage/Current wave form at V1

SIMULATION

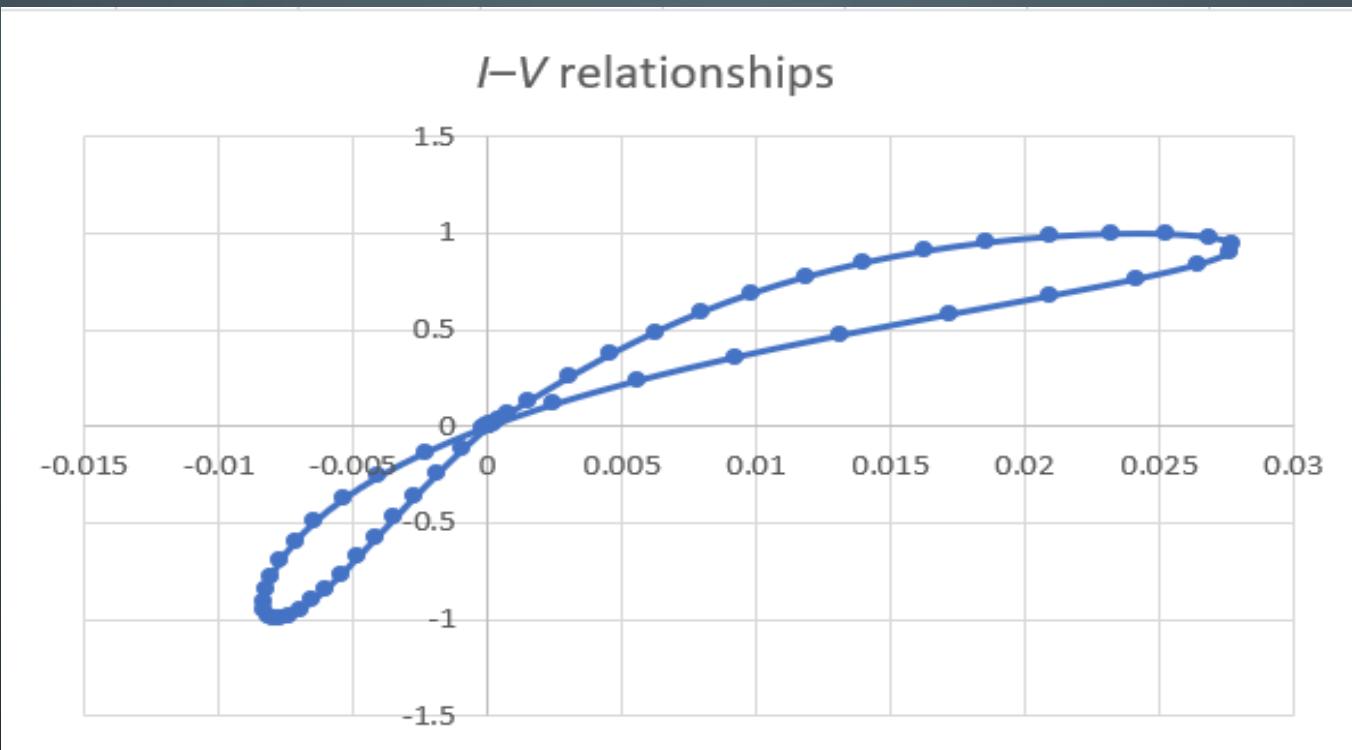


“If it’s pinched, it’s a memristor” – Chua, Leon


ACTUAL

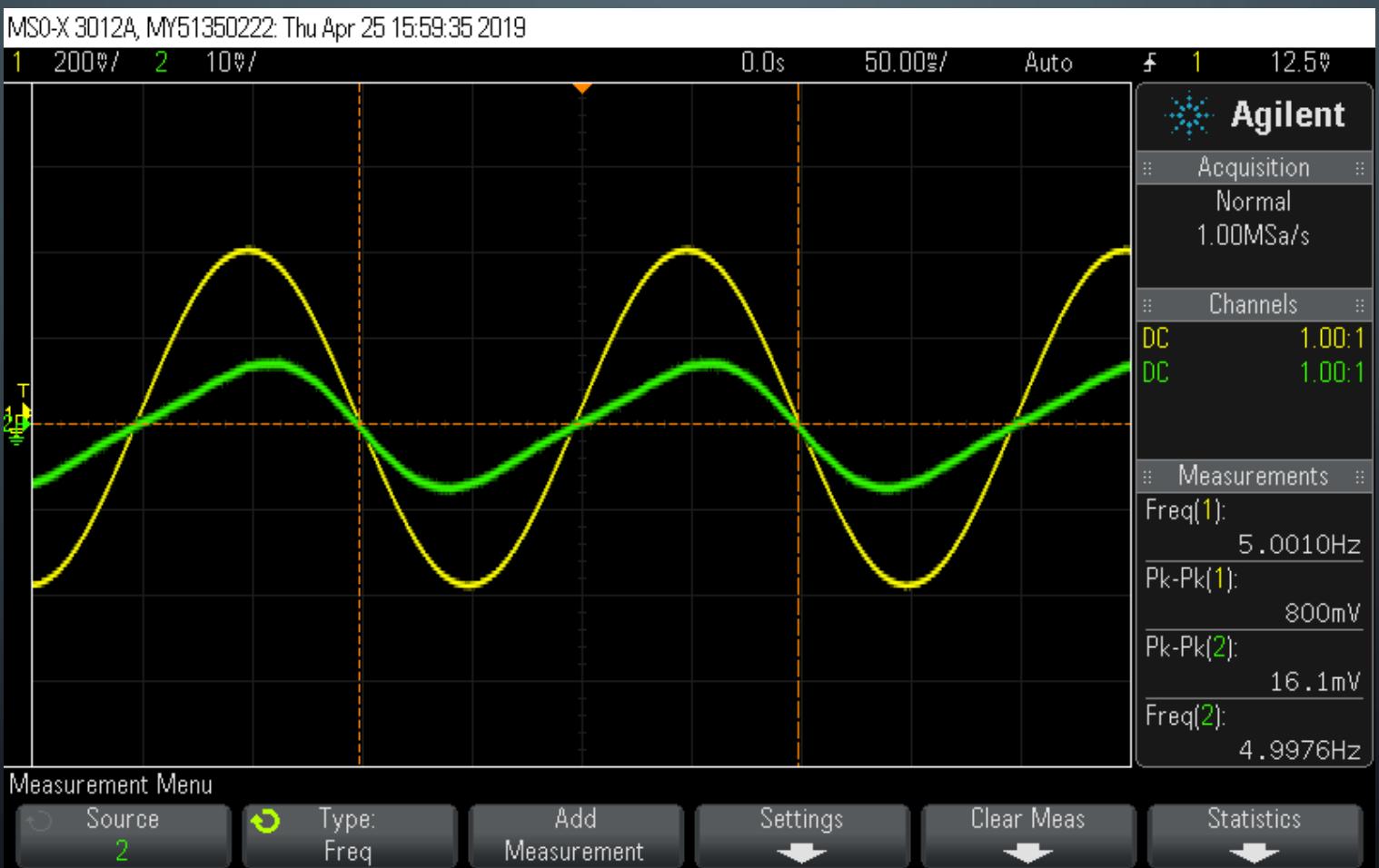


ACTUAL

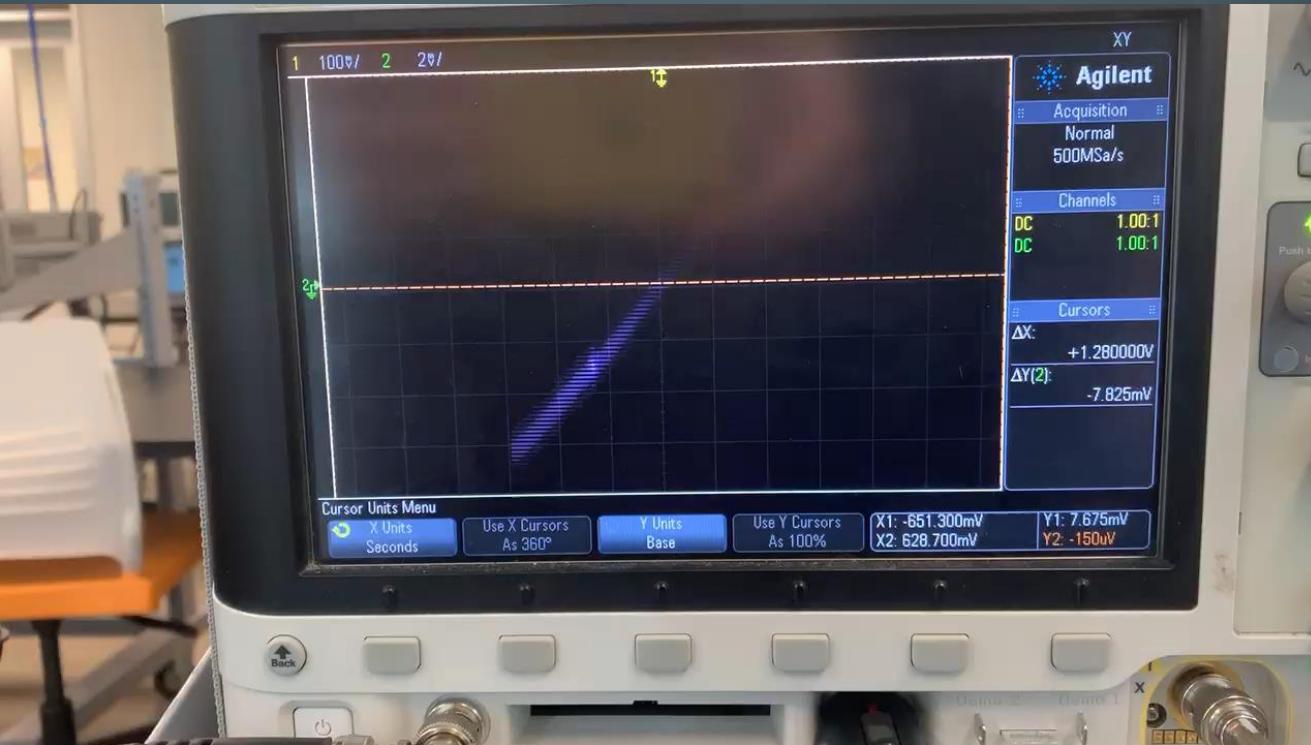


ACTUAL

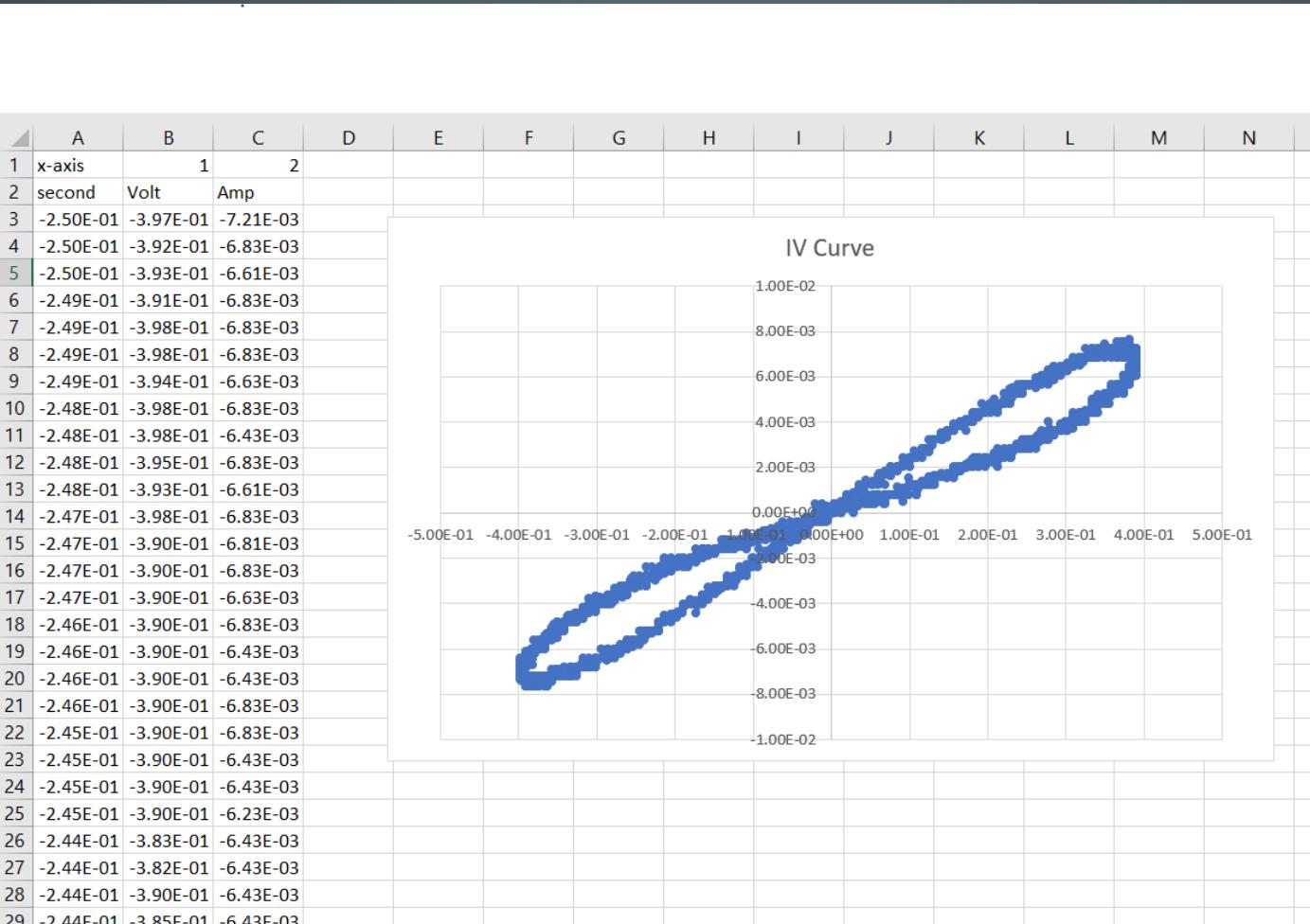

ACTUAL

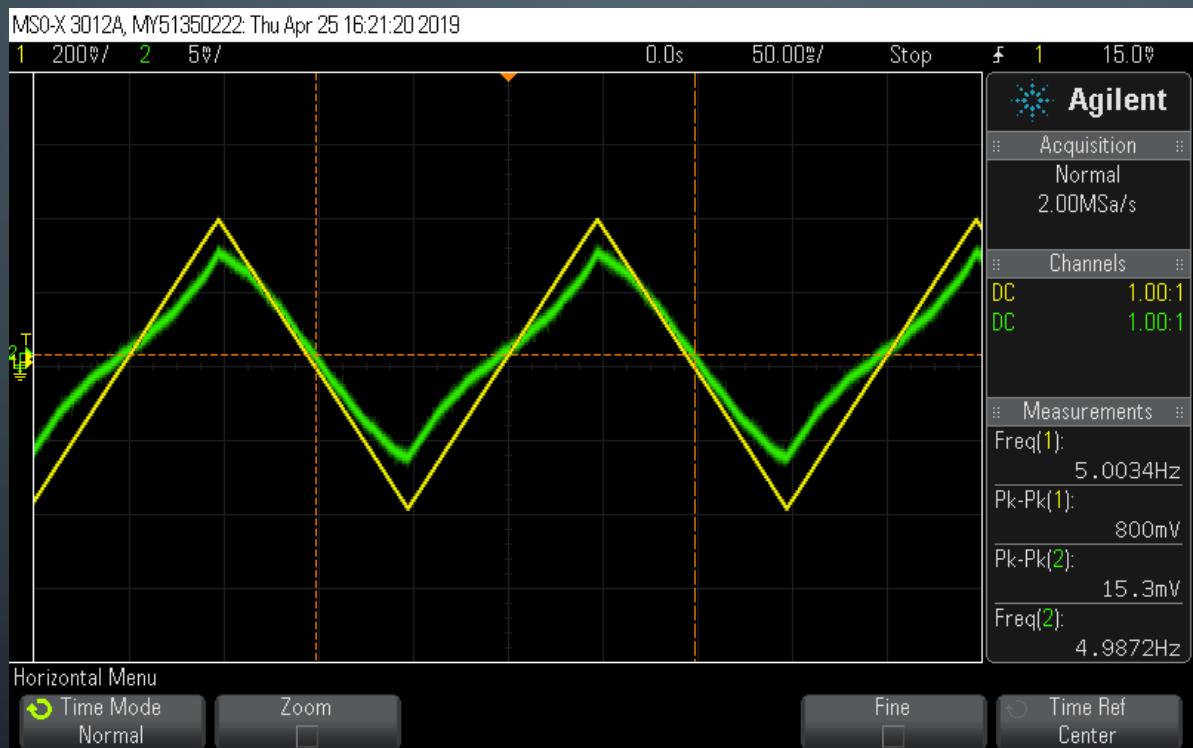


ACTUAL

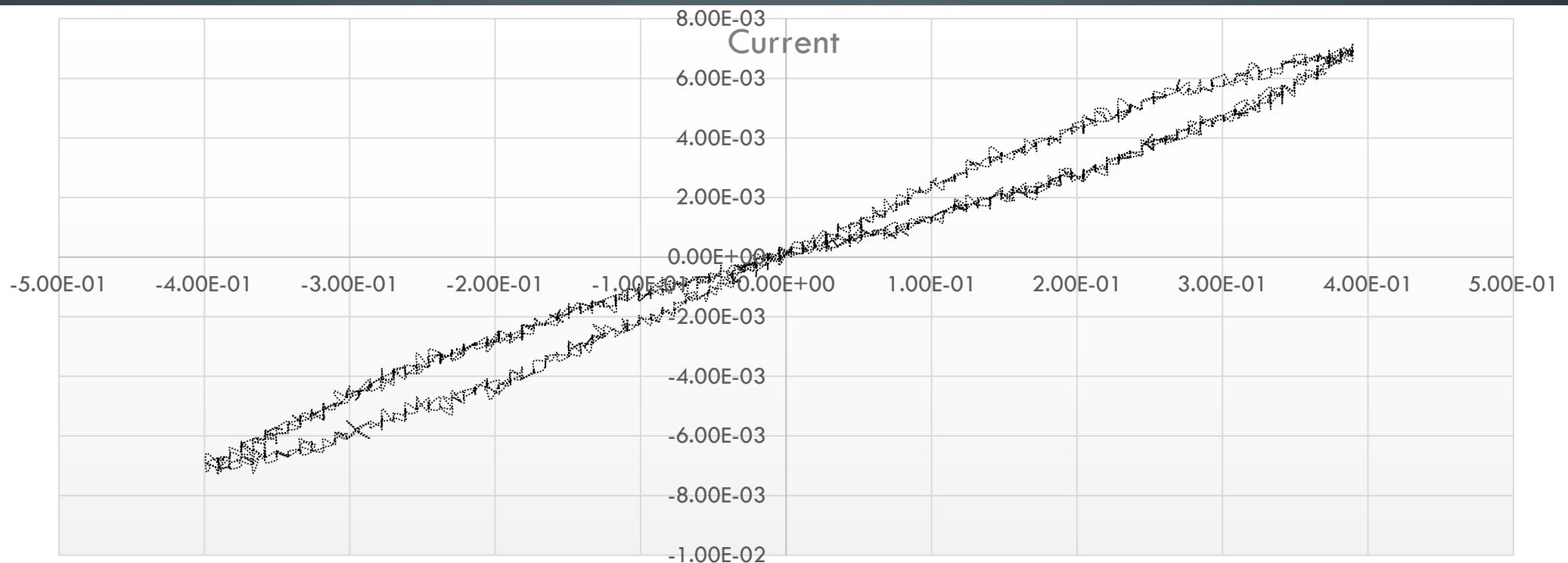

REFERENCE

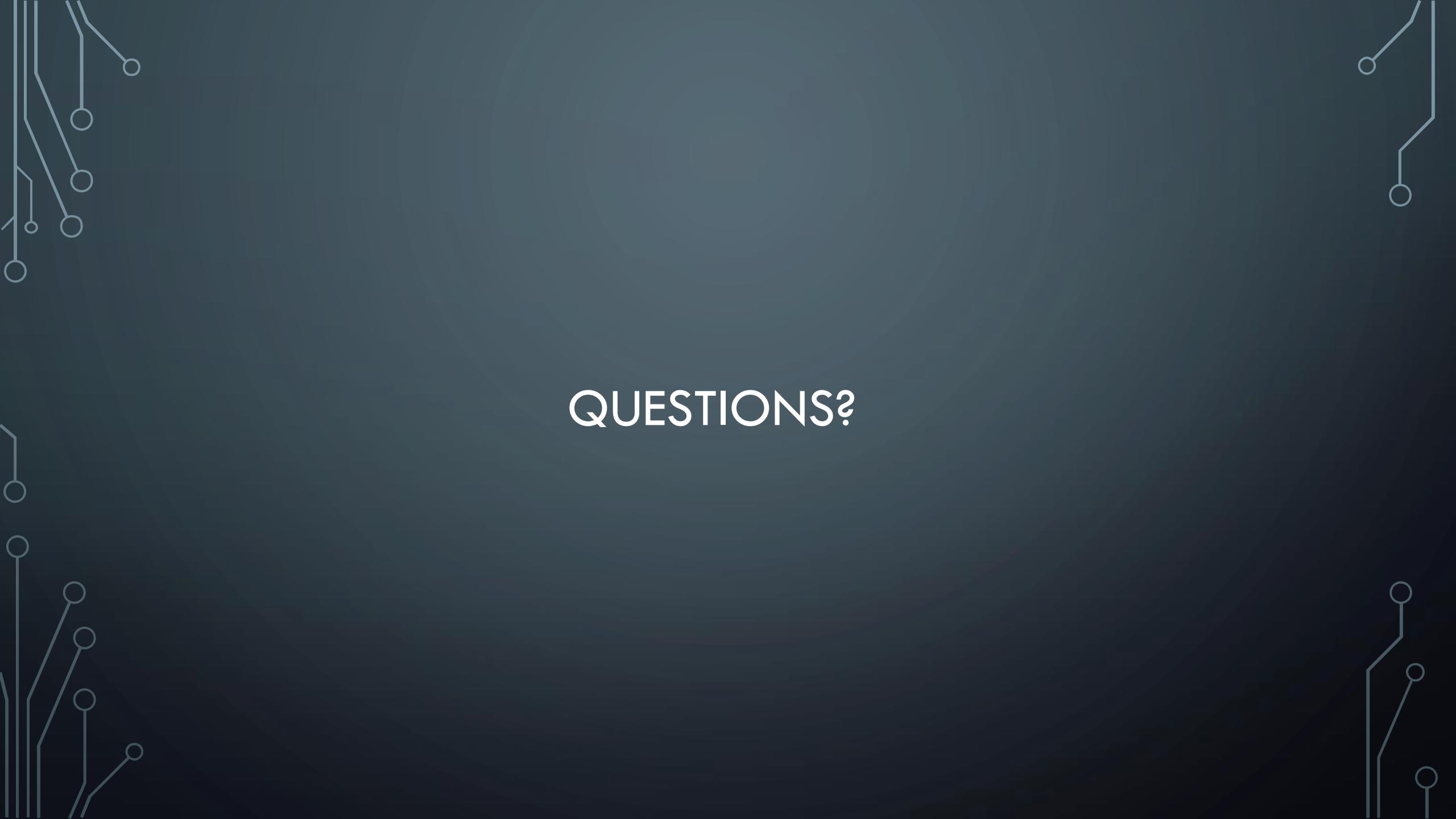- Xiao-Yuan, Wang, et al. "Implementation of an analogue model of a memristor based on a light-dependent resistor." *Chinese Physics B* 21.10 (2012): 108501



QUESTIONS?